

Logic Design (continued)

XOR Revisited

XOR is also called **modulo-2** addition.

| A | B | C | F |
|---|---|---|---|
| 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 1 |
| 0 | 1 | 0 | 1 |
| 0 | 1 | 1 | 0 |
| 1 | 0 | 0 | 1 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 0 |
| 1 | 1 | 1 | 1 |


$A \oplus B = 1$ only when there are an odd number of 1's in (A,B). The same is true for $A \oplus B \oplus C$ also.

$$\left. \begin{array}{l} 1 \oplus A = \overline{A} \\ 0 \oplus A = A \end{array} \right\}$$

Why?

Logic Design Examples


Half Adder

 


$$S = A \oplus B$$

$$C = A.B$$

| A | B | S | C |
|---|---|---|---|
| 0 | 0 | 0 | 0 |
| 0 | 1 | 1 | 0 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 1 |

 

Full Adder

 

| A | B | C _{in} | S | C _{out} |
|---|---|-----------------|---|------------------|
| 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 1 | 0 |
| 0 | 1 | 0 | 1 | 0 |
| 0 | 1 | 1 | 0 | 1 |
| 1 | 0 | 0 | 1 | 0 |
| 1 | 0 | 1 | 0 | 1 |
| 1 | 1 | 0 | 0 | 1 |
| 1 | 1 | 1 | 1 | 1 |


$$S = A \oplus B \oplus C_{in}$$

$$C_{out} = A.B + B.C_{in} + A.C_{in}$$

 Question. Can you design a full adder using two half-adders (and a few gates if necessary)?

Decoders

A typical decoder has n inputs and 2^n outputs.



A 2-to-4 decoder and its truth table

$$\begin{aligned} D3 &= A.B \\ D2 &= A.\bar{B} \\ D1 &= \bar{A}.B \\ D0 &= \bar{A}.\bar{B} \end{aligned}$$

Draw the circuit of this decoder.


The decoder works per specs when (**Enable = 1**). When **Enable = 0**, all the outputs are 0.

Exercise. Design a 3-to-8 decoder.

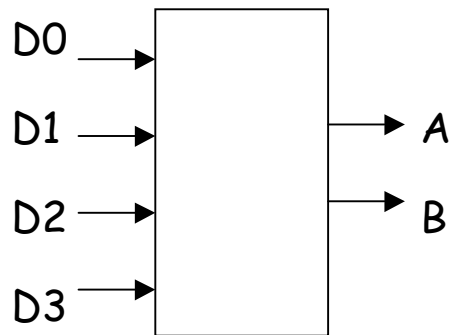Question. Where are decoders used?

Encoders

A typical encoder has 2^n inputs and n outputs.




| D0 | D1 | D2 | D3 | A | B |
|----|----|----|----|---|---|
| 1 | 0 | 0 | 0 | 0 | 0 |
| 0 | 1 | 0 | 0 | 0 | 1 |
| 0 | 0 | 1 | 0 | 1 | 0 |
| 0 | 0 | 0 | 1 | 1 | 1 |

A 4-to-2 encoder and its truth table


$$A = D1 + D3$$
$$B = D2 + D3$$

Multiplexor

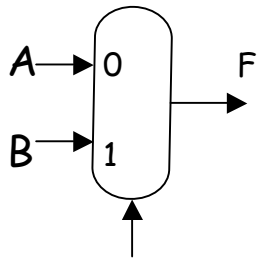It is a **many-to-one switch**, also called a **selector**.



Control S

 

Specifications of the mux

A 2-to-1 mux

$$F = \overline{S} \cdot A + S \cdot B$$

Exercise. Design a 4-to-1 multiplexor using two 2-to-1 multiplexors.