 


A 1-bit ALU




Understand how this circuit works.

Then look at the diagram of the 32-bit ALU in p.235.

Need to add one more input to the mux to implement **slt**

Converting an adder into a subtractor

 - $A - B$ (here - means arithmetic subtraction)
= $A + 2$'s complement of B
= $A + 1$'s complement of $B + 1$




1-bit adder/subtractor

For subtraction, B invert = 1 and $Carry\ in = 1$

1-bit ALU for MIPS

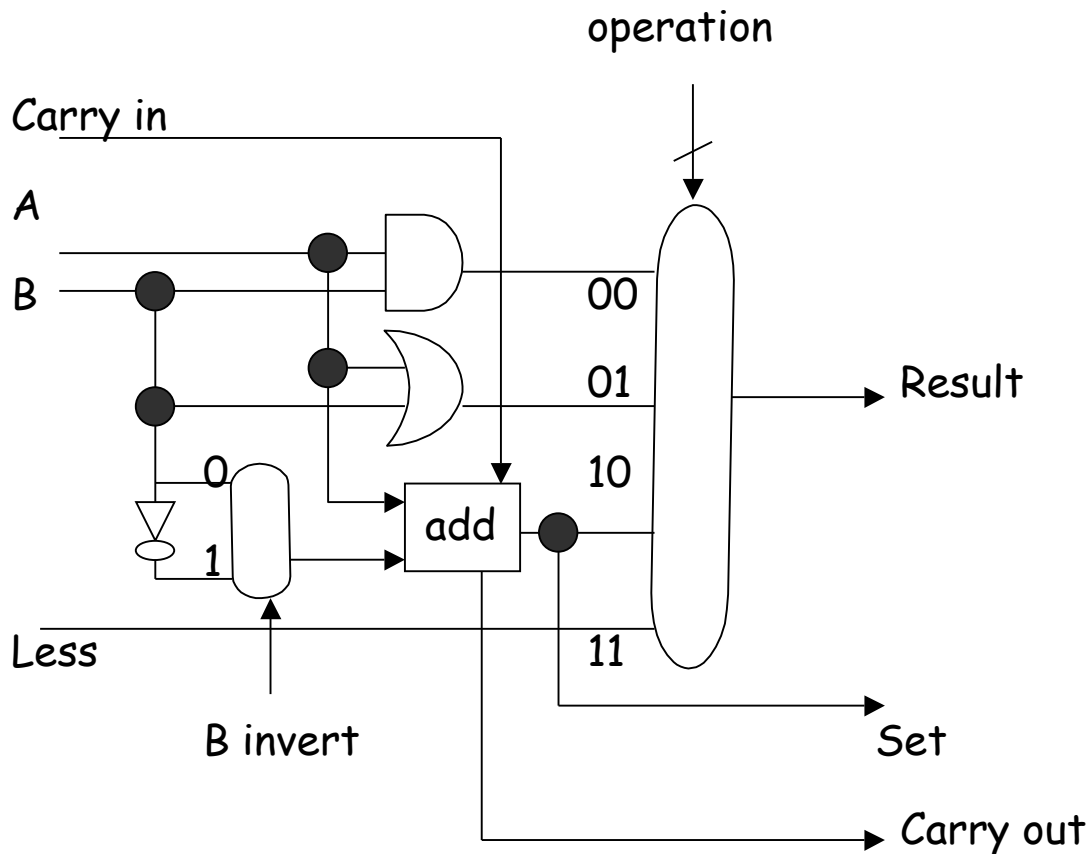
Assume that it has the instructions add, sub, and, or, slt.



Less will be used to detect if the **32-bit number** A is less than the **32-bit number** B. See the next page.

If $A < B$ then Set = 1 else Set = 0

A 32-bit ALU for MIPS

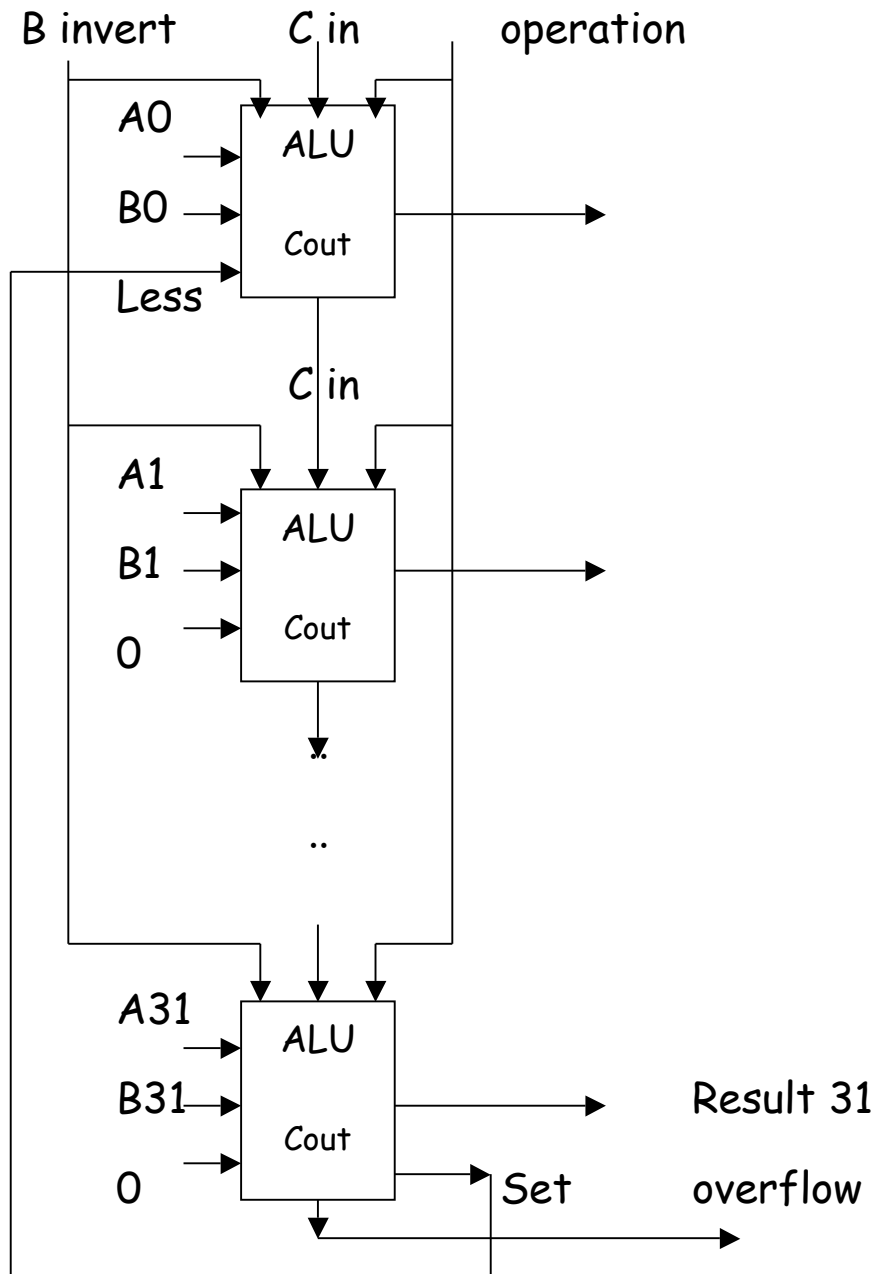

Fast Carry Propagation

During addition, the carry can trigger a "ripple" from the LSB to the MSB. This slows down the speed of addition.

$\begin{array}{r} 01111111111111111111 \\ + \\ 000000000000000001 \end{array}$
--

How to overcome this? Consider the following:

$$\begin{aligned} c_1 &= a_0.b_0 + a_0.c_0 + b_0.c_0 \\ &= a_0.b_0 + (a_0 + b_0).c_0 \\ &= g_0 + p_0.c_0 \quad (\text{where } g_0 = a_0.b_0, p_0 = a_0 + b_0) \end{aligned}$$

$$\begin{aligned} c_2 &= a_1.b_1 + (a_1 + b_1).c_1 \\ &= g_1 + p_1.(g_0 + p_0.c_0) \\ &= g_1 + p_1.g_0 + p_1.p_0.c_0 \end{aligned}$$

$$c_4 = g_3 + p_3.g_2 + p_3.p_2.g_1 + p_3.p_2.p_1.g_0 + p_3.p_2.p_1.p_0.c_0$$

$c_{32} = ?$

It will be complex. But you can use a two-level circuit to generate c_4 . This will expedite addition. But it is impractical due to the complexity.

Practical circuits use a two-phase approach. See the example of the 16-bit adder, designed from four 4-bit adders in p.246. Let

$$G_0 = g_3 + p_3.g_2 + p_3.p_2.g_1 + p_3.p_2.p_1.g_0$$

$$G_1 = g_7 + p_7.g_6 + p_7.p_6.g_5 + p_7.p_6.p_5.g_4$$

$$G_2 = g_{11} + p_{11}.g_{10} + p_{11}.p_{10}.g_9 + p_{11}.p_{10}.p_9.g_8$$

$$G_3 = g_{15} + p_{15}.g_{14} + p_{15}.p_{14}.g_{13} + p_{15}.p_{14}.p_{13}.g_{12}$$

$$P_0 = p_3.p_2.p_1.p_0$$

$$P_1 = p_7.p_6.p_5.p_4$$

$$P_2 = p_{11}.p_{10}.p_9.p_8$$

$$P_3 = p_{15}.p_{14}.p_{13}.p_{12}$$

Then

$$C1 = G0 + P0.c0$$

$$C2 = G1 + P1.G0 + P1.P0.c0$$

$$C3 = G2 + P2.G1 + P2.P1.G0 + P2.P1.P0.c0$$

$$C4 = G3 + P3.G2 + P3.P2.G1 + P3.P2.P1.G0 + P3.P2.P1.P0.c0$$

This is implemented in the **carry look-ahead adder**.

See the figure in p. 246 of your textbook.

How much faster is the carry look-ahead adder?

Multiplication

Be familiar with shift operations first

0 1 1 1 0 1 0 0

1 0 1 0 0 0 1 1

Shift right 

 shift left

0 0 1 1 1 0 1 0

0 1 0 0 0 1 1 1


$$\begin{array}{r} 1\ 0\ 0\ 1 \quad (\text{multiplicand}) \\ 0\ 1\ 0\ 1 \quad (\text{multiplier}) \\ \hline 1\ 0\ 0\ 1 \\ 0\ 0\ 0\ 0 \\ 1\ 0\ 0\ 1 \\ 0\ 0\ 0\ 0 \\ \hline 0\ 1\ 0\ 1\ 1\ 0\ 1 \end{array}$$

See the diagrams in page 254 and 255 of your textbook, and learn how a multiplier works.

Floating point representation

A scheme for representing a number **very small** to **very large**.

 It is widely used in the scientific world. Consider, the floating point number



In **decimal** it means $(+/-) 1. \text{yyyyyyyyyyyy} \times 10^{\text{xxxx}}$

In **binary**, it means $(+/-) 1. \text{yyyyyyyyyyyy} \times 2^{\text{xxxx}}$

(The 1 is implied)

IEEE 754 representation



$$\text{Largest} = 1.111... \times 2^{+127} \quad \square \quad 2 \times 10^{+38}$$

$$\text{Smallest} = 1.000 ... \times 2^{-128} \quad \square \quad 1 \times 10^{-38}$$

These can be positive and negative, depending on s.

IEEE 754 double precision (64 bits)

S	exponent	significand
---	----------	-------------

1 11 bits 52 bits

Largest = $1.111... \times 2^{+1023}$

Smallest = $1.000... \times 2^{-1024}$

What do you mean by **overflow** and **underflow** in FP?

An overflow occurs when the number is **too large to fit** in the frame. An underflow occurs when the number **is too small to fit** in the given frame.

Floating Point Addition

Example using decimal

$$A = 9.999 \times 10^1, B = 1.610 \times 10^{-1}, A+B = ?$$

Step 1. Align the smaller exponent with the larger one.

$$B = 0.0161 \times 10^1 = 0.016 \times 10^1 \text{ (round off)}$$

Step 2. Add significands

$$9.999 + 0.016 = 10.015, \text{ so } A+B = 10.015 \times 10^1$$

Step 3. Normalize

$$A+B = 1.0015 \times 10^2$$

Step 4. Round off

$$A+B = 1.002 \times 10^2$$

Now, try to add 0.5 and -0.4375 in binary.

Floating Point Multiplication

Example using decimal

$$A = 1.110 \times 10^{10}, B = 9.200 \times 10^{-5} \quad A \times B = ?$$

Step 1. Exponent of $A \times B = 10 + (-5) = -5$

Step 2. Multiply significands

$$1.110 \times 9.200 = 10.212000$$

Step 3. Normalize the product

$$10.212 \times 10^{-5} = 1.0212 \times 10^{-5}$$

Step 4. Round off

$$A \times B = 1.021 \times 10^{-5}$$

Step 5. Decide the sign of $A \times B$ ($+ \times + = +$)

$$\text{So, } A \times B = + 1.021 \times 10^{-5}$$

Now try to multiply 0.5 with -0.4375 in binary. Use IEEE 754 format.